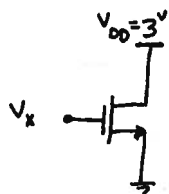


Chapter 2

2.1) a) NMOS :




for $V_x < V_{TH} (= 0.7)$ device is off, $I_D \approx 0$

for $V_x \geq 0.7$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_x - 0.7)^2 (1 + \lambda \cdot 3V) \quad (L_{eff} = 0.5 \mu - 2L_D)$$
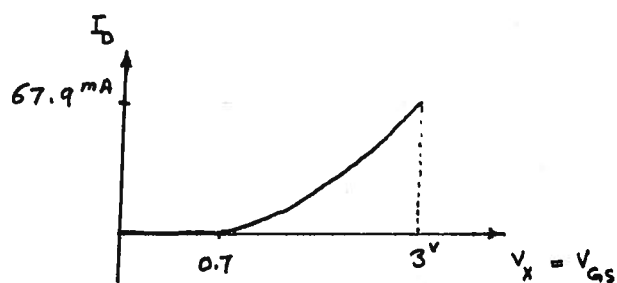
$$I_D = 12.8 \left(\frac{mA}{V^2} \right) \cdot (V_x - 0.7)^2$$



b) PMOS :

Solution is the same

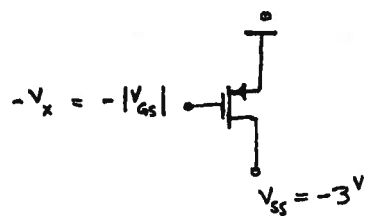


for $|V_{GS}| < V_{TH} (= 0.8)$ $I_D \approx 0$

for $|V_{GS}| \geq 0.8$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L_{eff}} (V_x - 0.8)^2 (1 + \lambda \cdot 3V)$$
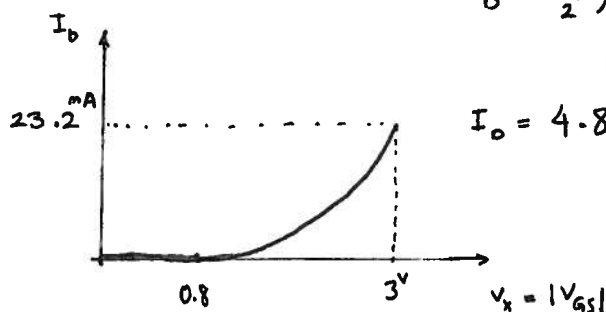
$$I_D = 4.8 \left(\frac{mA}{V^2} \right) \cdot (V_x - 0.8)^2$$



2.2) a) NMOS

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 3.66 \frac{mA}{V} \quad (\text{Neglecting } L_D)$$

$$r_o = \frac{1}{\lambda I_D} = 20 \text{ k}\Omega$$

$$\text{Intrinsic gain} = g_m r_o = 733 \frac{V}{V}$$

b) PMOS

$$g_m = \sqrt{2\mu_p C_{ox} \frac{W}{L} I_D} = 1.96 \frac{mA}{V}$$


$$r_o = \frac{1}{\lambda I} = \frac{1}{0.2 \cdot 0.5 \text{ mA}} = 10 \text{ k}\Omega$$

$$g_m r_o = 19.6 \frac{V}{V}$$

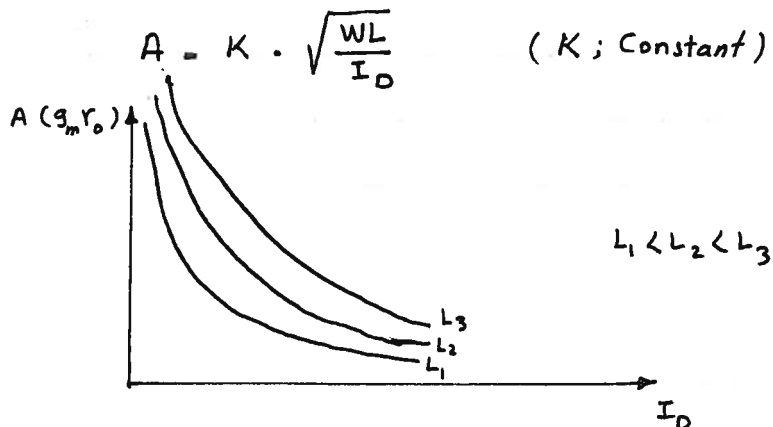
2.3) $g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D}$ $r_o = \frac{1}{\lambda I_D}$ Assume $\lambda = \frac{d}{L}$

$$A = g_m r_o = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \cdot \frac{L}{\alpha I_D}$$

$$A = K \cdot \sqrt{\frac{WL}{I_D}} \quad (K; \text{Constant})$$



2.4)

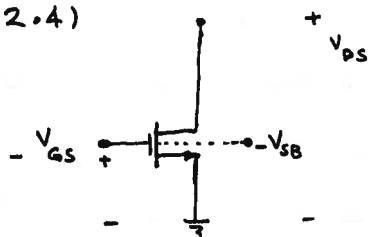

I_D versus V_{GS} : (for NMOS)



I) for $V_{GS} < V_{TH}$, $I_D \approx 0$

II) for $V_{TH} < V_{GS} < V_{TH} + V_{DS}$ $\Rightarrow$ Device is in the Saturation region

$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

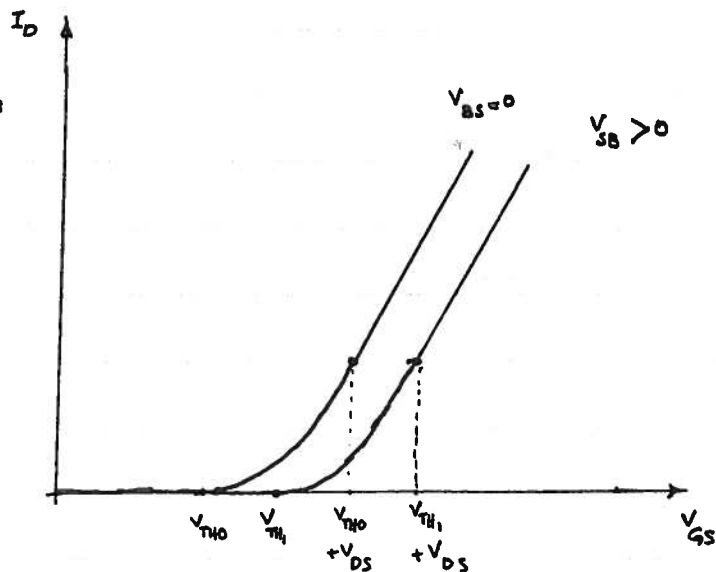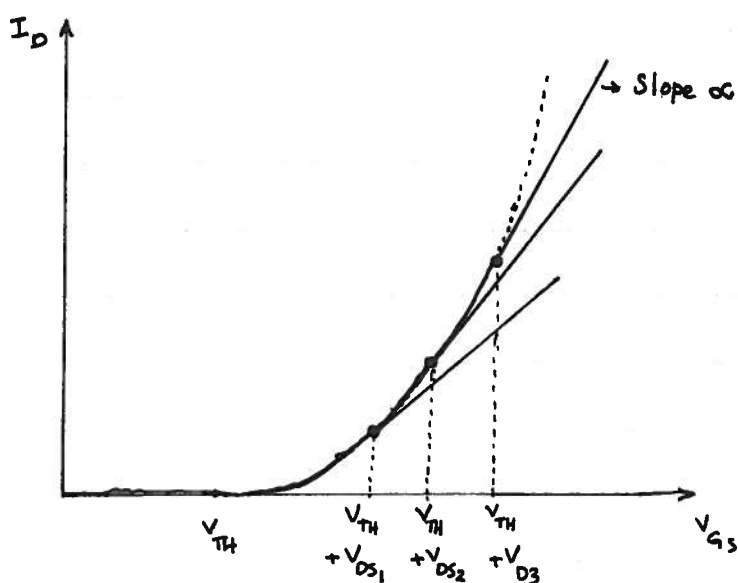
III) for $V_{GS} > V_{TH} + V_{DS}$ $\Rightarrow$ Device operates in the triode region

$$I_D \approx \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$



Changing V_{SB} just shifts the curve to the right for $V_{SB} > 0$ or to the left for $V_{SB} < 0$

2.5) a)

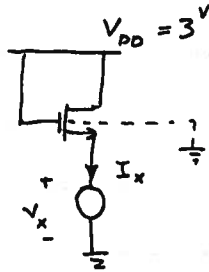

$$\lambda = 0.1, \gamma = 0.45, 2\phi_F = 0.9, V_{TH0} = 0.7$$

$$V_{GS} = 3 - V_x, \quad V_{DS} = 3 - V_x, \quad V_{SB} = V_x$$

$$V_{TH} = V_{TH0} + \gamma (\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$


$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (3 - V_x - 0.7 - 0.45(\sqrt{0.9 + V_x} - \sqrt{0.9}))^2 (1 + \lambda(3 - V_x))$$

The above equation is valid for


$$3 - V_x - 0.7 - 0.45(\sqrt{0.9 + V_x} - \sqrt{0.9}) > 0, \quad \text{i.e. } V_x < 1.97 \text{ V}$$

$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (2.727 - V_x - 0.45\sqrt{0.9 + V_x})^2 (1.3 - 0.1V_x)$$

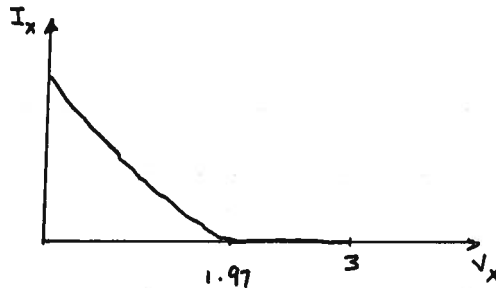
$$\text{and } I_x = 0 \quad \text{for } 1.97 < V_x$$


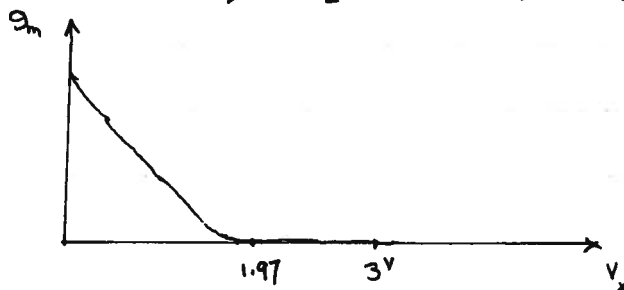
$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_x}$$



2.5) b,

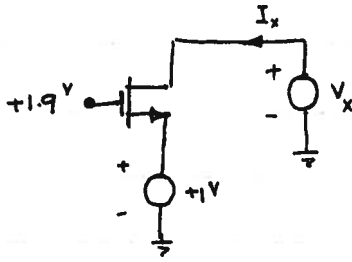

$$\lambda = \gamma = 0 \quad V_{TH} = 0.7$$

for $0 < V_x < 1$, S and D exchange their roles.

$$V_{GS} = 1.9 - V_x \quad V_{DS} = 1 - V_x, \quad V_{DD} = 1.2 - V_x$$

$$I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[(1.2 - V_x) \times 2 \times (1 - V_x) - (1 - V_x)^2 \right]$$

$$I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (1 - V_x) (1.4 - V_x)$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{DS} = \mu_n C_{ox} \frac{W}{L} (1 - V_x) \text{ (absolute value)}$$

The above equations are valid for $V_x < 1$

Then the direction of current is reversed.

$$V_{GS} = 1.9 - 1 = 0.9 \quad V_{DS} = V_x - 1, \quad V_{DD} = 0.9 - 0.7 = 0.2$$

for $V_x < 1.2$, device operates in the triode region.

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[2 \times 0.2 \times (V_x - 1) - (V_x - 1)^2 \right]$$



$$g_m = \mu_n C_{ox} \frac{W}{L} (V_x - 1)$$

for $V_x > 1.2$, Device goes into saturation region


2.5) b Cont

$$\text{So, } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.2)^2 ,$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (0.2)$$

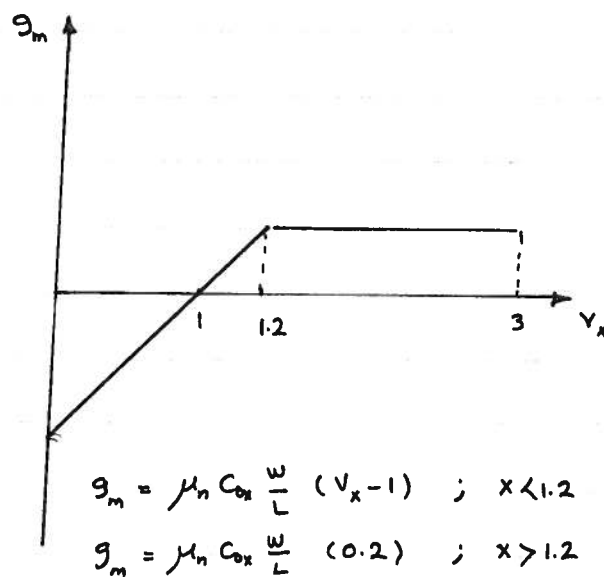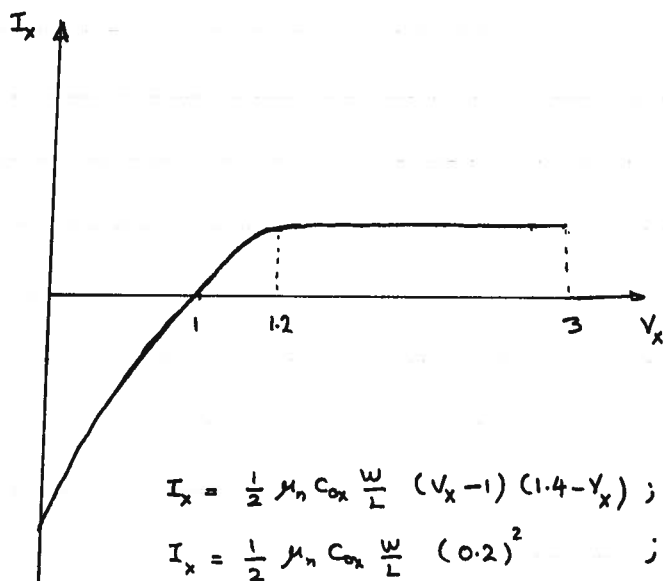

2.5) c

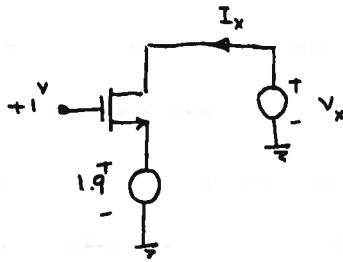

$$\lambda = \gamma = 0$$

$$V_{TH} = 0.7$$

S and D exchange their roles.

$$V_{GS} = 1 - V_x$$

$$V_{DS} = 1.9 - V_x$$

$$V_{OD} = V_{GS} - V_{TH} = 0.3 - V_x$$

Device is in Saturation region, So, $I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.3 - V_x)^2$

Device turns off when $V_x = 0.3$ and never turns on again.

$$\text{So, } I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.3 - V_x)^2 ; x < 0.3$$



$$I_x = 0$$

; otherwise


$$\text{Then } g_m = -\mu_n C_{ox} \frac{W}{L} (0.3 - V_x) ; x < 0.3$$

$$g_m = 0$$

; otherwise

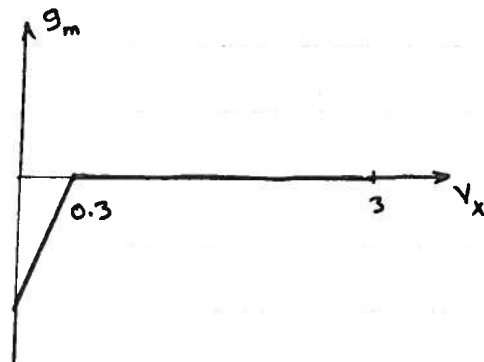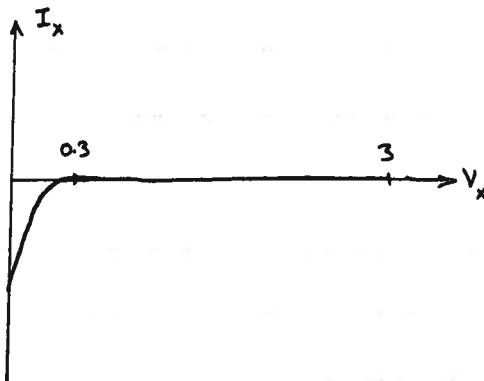

2.5) d)

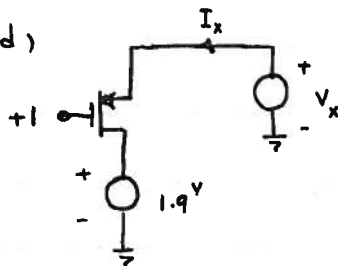

$$V_{TH} = -0.8 \quad \gamma = 0$$

D and S exchange their roles.

$$V_{GS} = -0.9 \quad V_{DS} = V_x - 1.9$$

for $V_x < 1.8$:

$$I_x = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$

Device remains in the saturation region until

$V_x = 1.9 - 0.1 = 1.8$, then device goes into the triode

region.

for $1.8 < V_x < 1.9$:

$$I_x = -\mu_p C_{ox} \frac{W}{L} \left[(-0.1)(V_x - 1.9) - \frac{1}{2} (V_x - 1.9)^2 \right]$$

$$g_m = +\mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$

for $V_x > 1.9$:

S and D exchange their roles again , when $V_x = 1.9$

for $V_x > 1.9$, Device operates in the triode region.

$$V_{GS} = 1 - V_x \quad , \quad V_{DS} = 1.9 - V_x$$

$$I_x = +\mu_p C_{ox} \frac{W}{L} \left[(1.8 - V_x)(1.9 - V_x) - \frac{1}{2} (1.9 - V_x)^2 \right]$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (1.9 - V_x)$$

$$2.5)d \quad 50; \quad 0 < V_x < 1.8$$



$$I_x = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$


$$1.8 < V_x < 3$$

$$I_x = +\mu_p C_{ox} \frac{W}{L} \times \frac{1}{2} (V_x - 1.9)(V_x - 1.7)$$
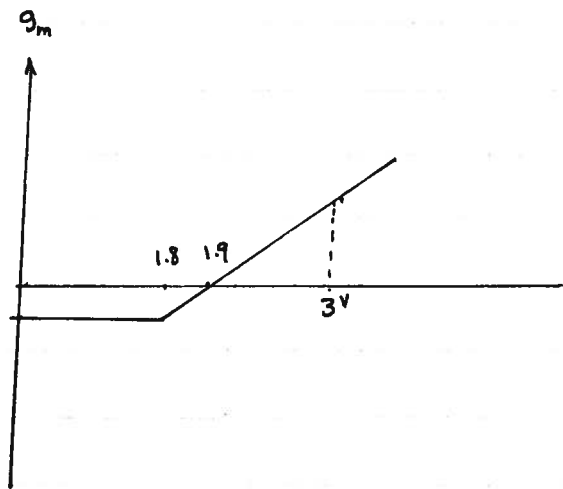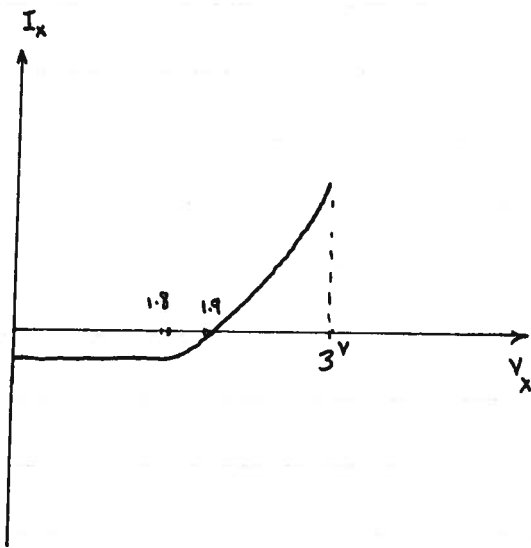
$$g_m = \mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$



2.5) e)

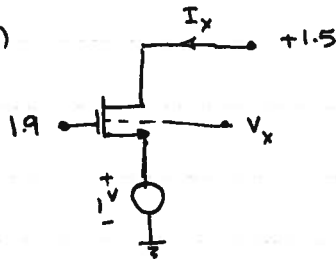

$$V_{TH0} = 0.7 \quad \gamma = 0.45 \quad 2\phi_f = 0.9 \quad , \lambda = 0$$

$$V_{SB} = 1 - V_x$$

$$V_{TH} = 0.7 + 0.45 (\sqrt{0.9 + 1 - V_x} - \sqrt{0.9})$$

$$V_{GS} = 0.9$$

$$V_{DS} = 0.5$$

for $V_x = 0$, $V_{TH} = 0.893$ So device is in saturation region.

$$\text{So } I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.2 - 0.45 (\sqrt{1.9 - V_x} - \sqrt{0.9}))^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (0.2 - 0.45 (\sqrt{1.9 - V_x} - \sqrt{0.9}))$$



These equations are valid upto the edge of triode region, i.e.

$$0.2 - 0.45 (\sqrt{1.9 - V_x} - \sqrt{0.9}) = 0.5 \Rightarrow V_x = 1.82$$


Above $V_x = 1.82$, device is in the triode region.

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2 \times 0.5 \times (0.2 - 0.45 (\sqrt{1.9 - V_x} - \sqrt{0.9})) - 0.5^2]$$

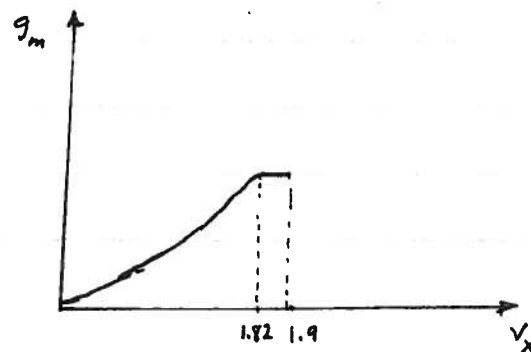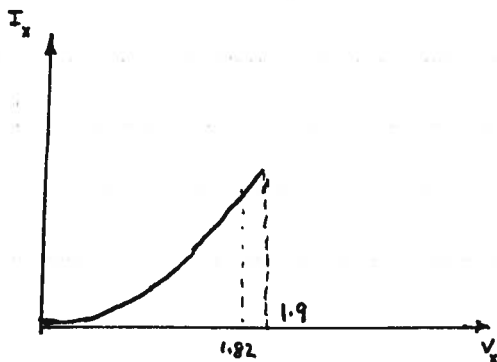$g_m = \mu_n C_{ox} \frac{W}{L} (0.5)$; This problem has been considered only for $0 < V_x < 1.9$ in which Schichman-Hodges Eq. is valid for V_{TH} .



2. ii) a)

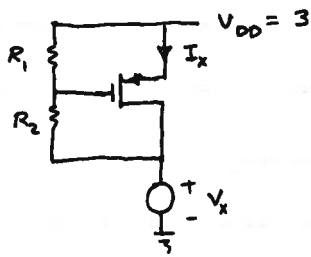

$$\gamma = 0$$

$$V_{SG} = (V_{DD} - V_X) \frac{R_1}{R_1 + R_2}$$



$$V_{SD} = V_{DD} - V_X$$

for $V_{SG} > |V_{TH}|$ Device is in the Saturation region (Device is

off; otherwise) $(V_{DD} - V_X) \frac{R_1}{R_1 + R_2} > -V_{TH}$

$$V_X < V_{DD} + V_{TH} \left(1 + \frac{R_2}{R_1}\right) \Rightarrow I_X = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[(V_{DD} - V_X) \frac{R_1}{R_1 + R_2} + V_{TH} \right]^2$$

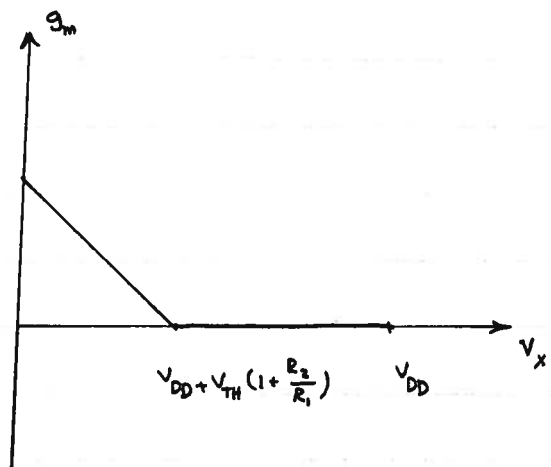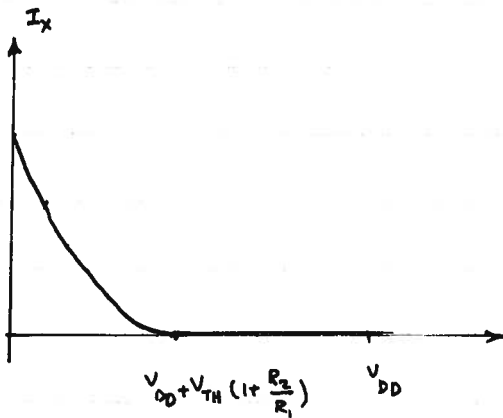
$$g_m = \mu_p C_{ox} \frac{W}{L} \left[(V_{DD} - V_X) \frac{R_1}{R_1 + R_2} + V_{TH} \right]$$



If $V_{DD} + V_{TH} \left(1 + \frac{R_2}{R_1}\right) < 0$ (e.g. for small value of R_1), device never

turns on!

2.6) b)

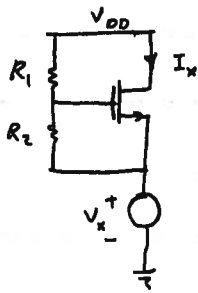

$$\gamma = 0$$

$$V_{GS} = (V_{DD} - V_x) \frac{R_2}{R_1 + R_2}$$



$$V_{DS} = V_{DD} - V_x$$

for $V_{GS} > V_{TH}$, Device is in the saturation region and


$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[(V_{DD} - V_x) \frac{R_2}{R_1 + R_2} - V_{TH} \right]^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} \left[(V_{DD} - V_x) \frac{R_2}{R_1 + R_2} - V_{TH} \right]$$

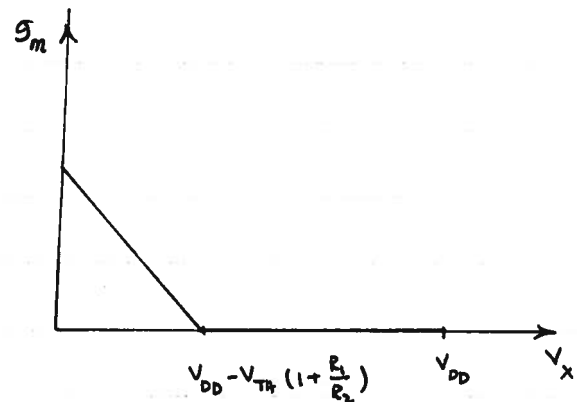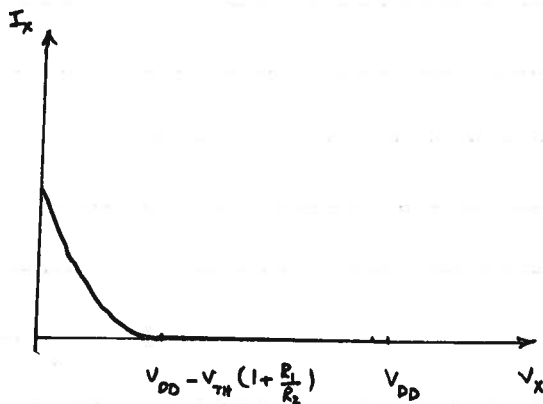for $V_x < V_{DD} - V_{TH} (1 + \frac{R_1}{R_2})$ (i.e. $V_{GS} > V_{TH}$)



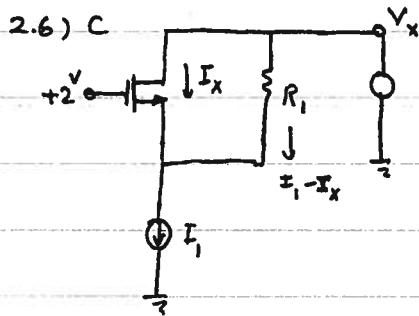If $V_{DD} - V_{TH} (1 + \frac{R_2}{R_1}) < 0$ device doesn't turn on.



I_x and $I_R = I_1 - I_x$ have the same polarity

So, $0 \leq I_x \leq I_1$

for $0 < V_x < 2 - V_{TH}$ (1.3) Device is in the triode.

$$V_{GS} = 2 - V_x + R_1 (I_1 - I_x) \quad , \quad V_{DS} = R_1 (I_1 - I_x)$$

$$I_x = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) - V_{DS}] V_{DS}$$

$$\Rightarrow (*) \quad I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [R_1 (I_1 - I_x) + 2(2 - V_{TH} - V_x)] [R_1 (I_1 - I_x)]$$

The above equation presents $I_x - V_x$ characteristics in this region.


In this region $g_m = \mu_n C_{ox} V_{DS} = \mu_n C_{ox} R_1 (I_1 - I_x)$


Then device enters the Saturation region; $V_{GS} = 2 - V_x + R_1 (I_1 - I_x)$

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2 - V_x + R_1 (I_1 - I_x) - V_{TH}]^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} [2 - V_x + R_1 (I_1 - I_x) - V_{TH}]$$

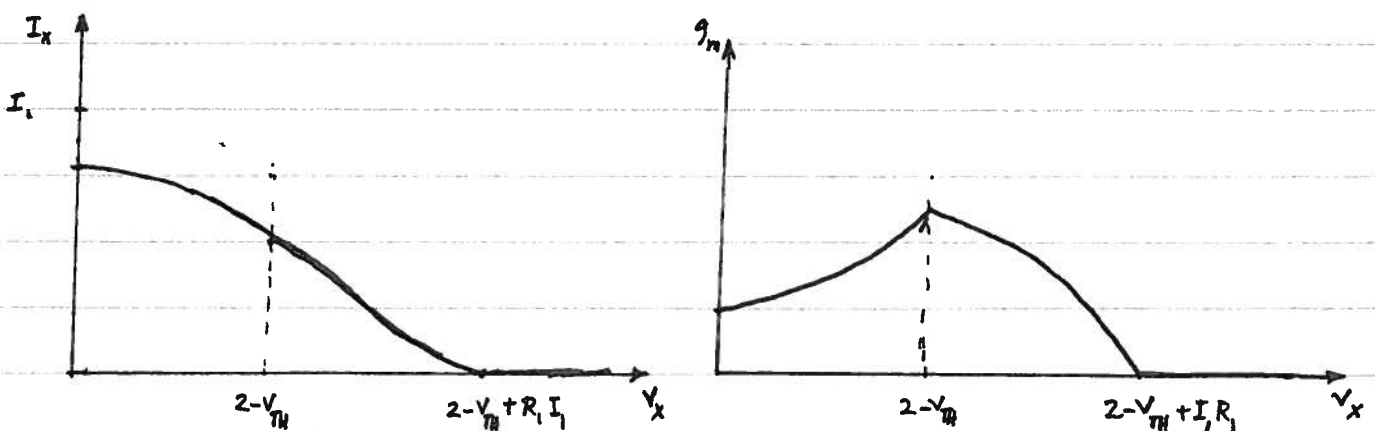Then device turns off when $V_x = 2 - V_{TH} + R_1 I_1$



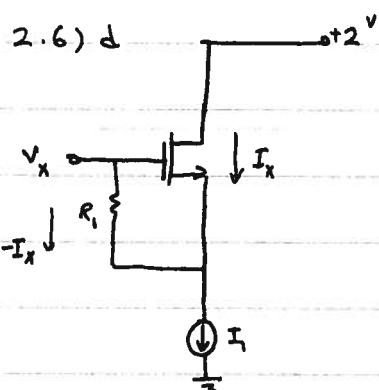

Assumption: $R_1 I_1 > V_{TH}$

for $0 < V_x < 2 + V_{TH}$: Device is in the saturation region

$$V_{GS} = R_1 (I_1 - I_x)$$

$$I_D = I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [R_1 (I_1 - I_x) - V_{TH}]^2$$

I_x is a constant that can be derived by solving the above equation.

Then device enters the triode region for $V_x > 2 + V_{TH}$

$$\text{In this case } V_{GS} = R_1 (I_1 - I_x) \quad V_{DS} = 2 - [V_x - R_1 (I_1 - I_x)] = 2 - V_x + R_1 (I_1 - I_x)$$

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2[R_1(I_1 - I_x) - V_{TH}] - 2 + V_x - R_1(I_1 - I_x)] \times (2 - V_x + R_1(I_1 - I_x))$$

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [(R_1(I_1 - I_x) - V_{TH}) + (V_x - 2 - V_{TH})][(R_1(I_1 - I_x) - V_{TH}) - (V_x - 2 - V_{TH})]$$

$$(*) \quad I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [(R_1(I_1 - I_x) - V_{TH})^2 - (V_x - 2 - V_{TH})^2]$$

The second term shows that I_x decreases when we increase V_x

The polarity of I_x changes for higher V_x (Device still is in triode)

(*) presents $I_x - V_x$ relationship in this region.