## Solutions to Lab Manual to accompany **Industrial Automated Systems:** Instrumentation and Motion Control

**Terry Bartelt** 



Australia • Brazil • Japan • Korea • Mexico • Singapore • Spain • United Kingdom • United States

## Experiment 1

# **Operational Amplifiers**

## **Experiment Questions**

- 1. analog
- 2. linear
- 3. greater
- 4. 6, -
- 5. –5V

INP		
<b>V</b> <sub>1</sub>	<b>V</b> 2	V <sub>OUT</sub> (V)
+4	+1	-5
+2	+3	+5
+1	0	-5
+4	+4	0
0	+1	+5
+3	+2	-5

V <sub>IN</sub> (V)	Vout(V)
+0.2	-1
-0.4	+2
0	0
+0.32	-1.6
0 +0.32	0 -1.6

V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)
+0.3	-0.75
-0.15	+0.38
-2.0	-5
+0.4	-1

Figure 1-2 b

Figure 1-3 b

Figure 1-3 c

Inp	ut Volt	age	Output Voltage					
<b>V</b> <sub>1</sub>	V <sub>2</sub>	V <sub>3</sub>	Measured	Calculated				
+1	+1	+1	-3	-3				
+1	-1	-1	+1	+1				
+2	-1	-1	0	0				
-3	-1	+3	+1	+1				
+1	+2	-1	-2	-2				

Figure 1-4 b



# **Schmitt Trigger**

#### **Procedure Question Answer**

1. No. Because the 7476 J-K flip-flop is negative-edge triggered, and reacts only to positive-to-negative–going signals that change abruptly. The rectified sine wave does not change fast enough.

#### Step 5

Point 1						
$V_{th} - =$	.9	_VDC				
$V_{th} + =$	1.7	_VDC				

Table 2-1

Waveform	At Point 1	At Point 2	Is the Flip-Flop Toggling (Yes, No)
Circuit (a)	$\sim$		NO
Circuit (b)			YES

#### Table 2-2

### **Experiment Questions**

- Convert electronic signals to square waves.
  Perform NAND gate and Inverter logic functions.
- 2. D
- 3. edge
- 4. Low, High
- 5. hysteresis
- 6. Because when sine waves are counted, they must be converted to square waves before being applied to a flip-flop.

#### Step 7

# **Magnitude Comparator**

Experiment

### **Procedure Question Answer**

1. If the high-order bits are equal, then the output state is determined by comparing the low-order bits.

### Step 2A

	Inp	ut B			Inp	ut A	Outputs			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	<b>A</b> 3	<b>A</b> 2	<b>A</b> 1	<b>A</b> 0	A <b< th=""><th>A=B</th><th>A&gt;B</th></b<>	A=B	A>B
0	0	0	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0	1	0	0
0	0	1	1	0	1	0	0	0	0	1
0	0	0	1	1	0	0	1	0	0	1

Table 3-2

#### Step 3B

	Input B Input A			Input A				nsion Ir	nputs		Outputs	5	
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	<b>A</b> 3	A <sub>2</sub>	<b>A</b> 1	<b>A</b> 0	I <sub>A</sub> <b< th=""><th>I<sub>A</sub>=B</th><th>IA&gt;B</th><th>A<b< th=""><th>A=B</th><th>A&gt;B</th></b<></th></b<>	I <sub>A</sub> =B	IA>B	A <b< th=""><th>A=B</th><th>A&gt;B</th></b<>	A=B	A>B
0	0	0	0	1	1	1	1	1	0	0	0	0	1
0	0	0	1	0	0	0	1	0	0	1	0	0	1
0	1	1	0	0	1	1	0	0	1	0	0	1	0
1	1	1	0	1	1	0	1	0	0	1	1	0	0
0	1	0	1	1	1	1	0	0	1	0	0	0	1

#### Table 3-4

## **Experiment Questions**

- 1. 1111
- 2. Yes. By connecting a Low to the MSB of inputs A and B, and applying the three binary bits to the remaining inputs.

3.  $I_A > B = 0$  $I_A = B = 0$  $I_A < B = 1$ 

4.4

5. When A is greater than B, or B is greater than A, the circuit would operate normally. When A is equal to B, however, output A<B would incorrectly go High instead of output A=B.



## **SCR Phase Control Circuit**

Step 3 169 volts, yes Step 4 15 volts, yes

- 1. D
- 2. B
- 3. 169–15 = 154
- 4. A
- 5. B
- 6. B



## Experiment 5

## **Photoresistor**

**Step 1** Dark resistance =  $40K\Omega$ 

**Step 3** Ambient light voltage = -8V Dark voltage = +7V

### **Design Question**

Switch the position of  ${\rm R}_1$  with that of the photoresistor.

- 1. A
- 2. B
- 3. B
- 4. B
- 5. A



## **Optocoupler**

Step 1 1 Meg ohm Step 2 150 ohms Step 4



### Step 5 B

Step 6 25KHz

**Step 7** I<sub>C</sub> = 3.5mA I<sub>f</sub> = 16mA CTR 22%

- 1. True
- 2. A
- 3. A
- 4. 25%
- 5. C

# **Digital-to-Analog Converter**

Experiment

### **Procedure Question Answers**

- 1. A
- 2. A
- 3. 16 (2<sup>4</sup>)
- 4. 1
- 5. Eight different voltage levels. When an open is at the LSB input, a binary 1 is always applied to the LSB digital input lead of the D/A converter. This causes the D/A converter to produce the following counts:

Desired Count	Count with Pin 12 Open
0	1
1	1
2	3
3	3
4	5
5	5
6	7
7	7
8	9
9	9
10	11
11	11
12	13
13	13
14	15
15	15

Full Download: http://alibabadownload.com/product/industrial-automated-systems-instrumentation-and-motion-control-1st-edition-bartelt-

8

Experiment 7 Digital-to-Analog Converter

6. 32

The number of outputs is determined by multiplying 2 by the power of the number of inputs applied to the digital input of the D/A converter  $(2^5)$ .

- 1. 256
- 2. 1
- 3. Change  $V_{REF}$  applied to pin 14.
  - Change the resistor value connected to pin 14.
  - Change the R<sub>F</sub> resistor connected to pin 4.